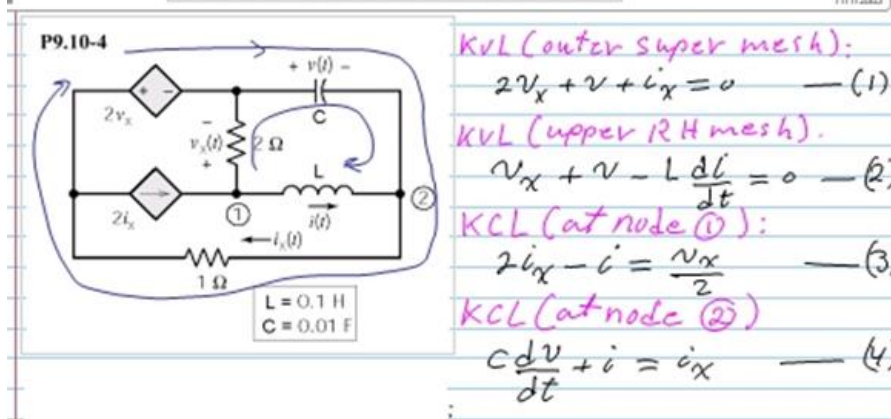


Solve the following circuit for  $v(t)$ ,  $t > 0$ .  
Assume  $v(0^-) = 10$  V and  $i(0^-) = 0$  A.



Given

$$2V_x + V + I_x = 0$$

Problem Using variable "I", so we use "I1"

$$V_x + V - \frac{1}{10} \cdot (s \cdot I1) = 0$$


$$2I_x - I1 = \frac{V_x}{2}$$

$$\frac{1}{100} \cdot (s \cdot V - 10) + I1 = I_x$$

$$U(s) := \text{Find}(V, V_x, I1, I_x) \rightarrow \begin{bmatrix} \frac{10}{3} \cdot \frac{(20 + 9 \cdot s)}{(40 \cdot s + 1000 + 3 \cdot s^2)} \\ -\frac{40}{3} \cdot \frac{(s + 5)}{(40 \cdot s + 1000 + 3 \cdot s^2)} \\ \frac{500}{(120 \cdot s + 3000 + 9 \cdot s^2)} \\ -\frac{10}{3} \cdot \frac{(s - 20)}{(40 \cdot s + 1000 + 3 \cdot s^2)} \end{bmatrix}$$


$$v(t) := U(s)_1 \text{ invlaplace, } s \rightarrow 10 \cdot \exp\left(\frac{-20}{3} \cdot t\right) \cdot \cos\left(\frac{10}{3} \cdot \sqrt{26} \cdot t\right) - \frac{20}{39} \cdot \exp\left(\frac{-20}{3} \cdot t\right) \cdot \sqrt{26} \cdot \sin\left(\frac{10}{3} \cdot \sqrt{26} \cdot t\right)$$
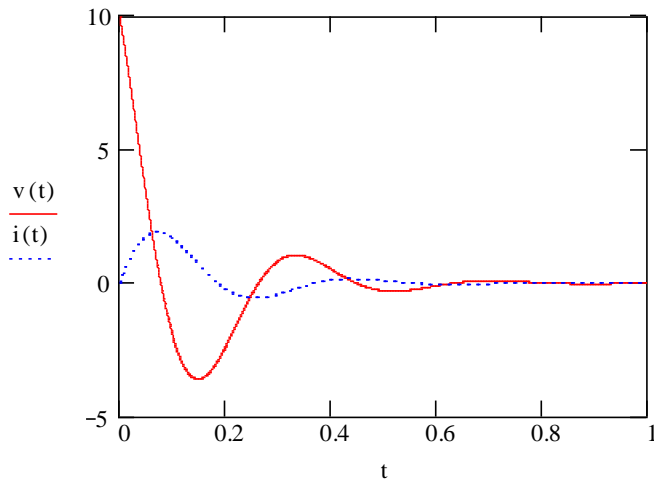
$$i(t) := U(s)_3 \text{ invlaplace, } s \rightarrow \frac{25}{39} \cdot \exp\left(\frac{-20}{3} \cdot t\right) \cdot \sqrt{26} \cdot \sin\left(\frac{10}{3} \cdot \sqrt{26} \cdot t\right)$$



### Example 2

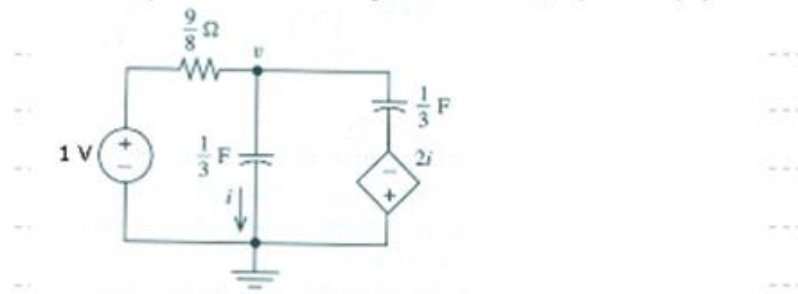III. Find  $v(t)$  for  $t > 0$  in the following circuit. Assume,  $v(0^+) = 0$  and  $i(0^-) = 0$ .



Given


$$\frac{8}{9} \cdot \left( V - \frac{1}{s} \right) + I1 + \frac{(V + 2I1) \cdot s}{3} = 0$$

$$I1 = \frac{1}{3} \cdot s \cdot V$$


$$U(s) := \text{Find}(V, I1) \rightarrow \begin{bmatrix} \frac{4}{s \cdot (4 + 3 \cdot s + s^2)} \\ \frac{4}{(12 + 9 \cdot s + 3 \cdot s^2)} \end{bmatrix}$$

$$v(t) := U(s)_1 \text{ invlaplace, } s \rightarrow 1 - \exp\left(\frac{-3}{2} \cdot t\right) \cdot \cos\left(\frac{1}{2} \cdot \sqrt{7} \cdot t\right) - \frac{3}{7} \cdot \exp\left(\frac{-3}{2} \cdot t\right) \cdot \sqrt{7} \cdot \sin\left(\frac{1}{2} \cdot \sqrt{7} \cdot t\right)$$

$$i(t) := U(s)_2 \text{ invlaplace, } s \rightarrow \frac{8}{21} \cdot \exp\left(\frac{-3}{2} \cdot t\right) \cdot \sqrt{7} \cdot \sin\left(\frac{1}{2} \cdot \sqrt{7} \cdot t\right)$$

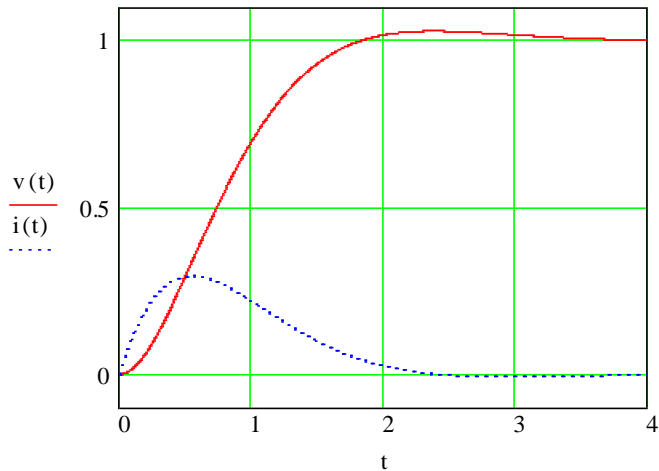

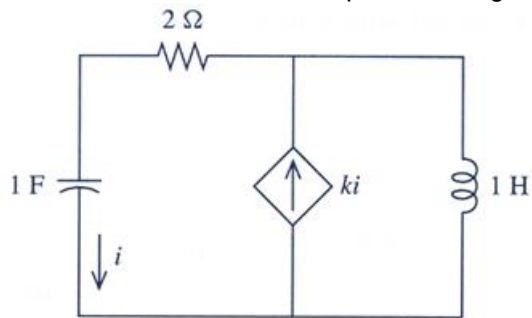Example 3: Solve for  $i(t)$ ,  $t > 0$ . Assume inductor current is zero at  $t=0$  and initial capacitor voltage is 1V. Set  $k = -2$ .



Given


$$s \cdot I_2 - V - 2I_1 = 0$$

$$s \cdot V - 1 = I_1$$


$$I_1 + I_2 = -2 \cdot I_1$$

$$U(s) := \text{Find}(V, I_1, I_2) \rightarrow \begin{bmatrix} \frac{(3 \cdot s + 2)}{(3 \cdot s^2 + 2 \cdot s + 1)} \\ -1 \\ \frac{3}{(3 \cdot s^2 + 2 \cdot s + 1)} \end{bmatrix}$$

$$i(t) := U(s)_2 \text{ invlaplace, } s \rightarrow \frac{-1}{2} \cdot \exp\left(\frac{-1}{3} \cdot t\right) \cdot \sqrt{2} \cdot \sin\left(\frac{1}{3} \cdot \sqrt{2} \cdot t\right)$$

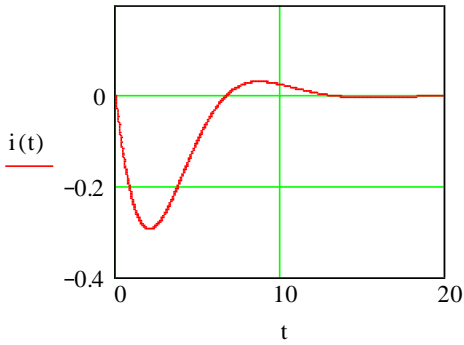

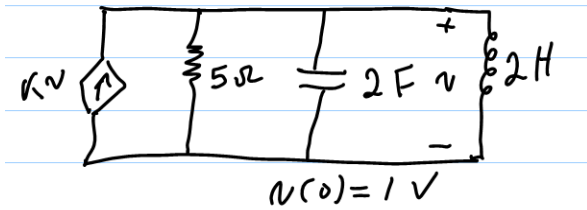Example 8: Find  $k$  so that  $v(t)$  is a pure sinusoid (i.e., circuit oscillates).



Given

$$\frac{V}{5} + 2s \cdot V - 2 + \frac{V}{2s} = k \cdot V$$

$$V(s, k) := \text{Find}(V) \rightarrow \frac{-20}{(-2 \cdot s - 20 \cdot s^2 - 5 + 10 \cdot k \cdot s)} \cdot s$$


Circuit Natural frequencies (poles):

$$-2 \cdot s - 20 \cdot s^2 - 5 + 10 \cdot k \cdot s = 0 \text{ solve, } s \rightarrow \left[ \begin{array}{l} \frac{-1}{20} + \frac{1}{4} \cdot k + \frac{1}{20} \cdot \left( -99 - 10 \cdot k + 25 \cdot k^2 \right)^{\frac{1}{2}} \\ \frac{-1}{20} + \frac{1}{4} \cdot k - \frac{1}{20} \cdot \left( -99 - 10 \cdot k + 25 \cdot k^2 \right)^{\frac{1}{2}} \end{array} \right]$$


For circuit to oscillate, we need zero real part for the natural frequencies, or  $k=1/5$ :

$$v(t) := V\left(s, \frac{1}{5}\right) \text{ invlaplace, } s \rightarrow \cos\left(\frac{1}{2} \cdot t\right)$$

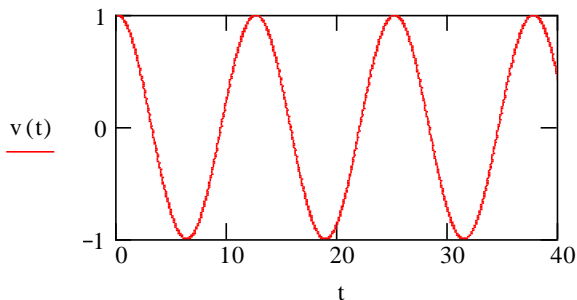As expected for a parallel LC circuit, the oscillation frequency is  $1/\sqrt{LC} = 1/2$



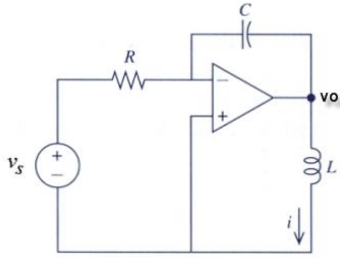Example 9: Solve for  $i(t)$  and  $v_o(t)$ ,  $t > 0$ . Assume that at  $t=0$ , the capacitor voltage is 1 volt and  $i(0) = 1$  amp. Let,  $v_s(t) = \sin(t)u(t)$ ,  $L=2H$ ,  $C=1/5F$  and  $R=10 \text{ Ohm}$ .



$$V_s(s) := \sin(t) \text{ laplace, } t \rightarrow \frac{1}{(s^2 + 1)}$$

Given



$$\frac{-s \cdot V_o - 1}{5} - \frac{V_s(s)}{10} = 0$$

$$V_o = 2s \cdot I_1 - 2$$


$$U(s) := \text{Find}(I_1, V_o) \rightarrow \left[ \begin{array}{l} \frac{1}{4} \cdot \frac{(4 \cdot s^3 + 4 \cdot s - 2 \cdot s^2 - 3)}{s^2 \cdot (s^2 + 1)} \\ \frac{-1}{2} \cdot \frac{(2 \cdot s^2 + 3)}{s \cdot (s^2 + 1)} \end{array} \right]$$

$$i(t) := U(s)_1 \text{ invlaplace, } s \rightarrow \frac{-3}{4} \cdot t + 1 + \frac{1}{4} \cdot \sin(t)$$


$$v_o(t) := U(s)_2 \text{ invlaplace, } s \rightarrow \frac{-3}{2} + \frac{1}{2} \cdot \cos(t)$$

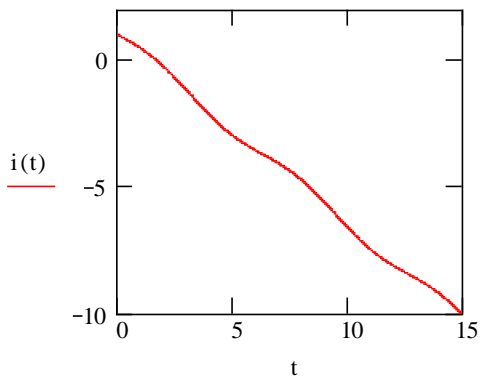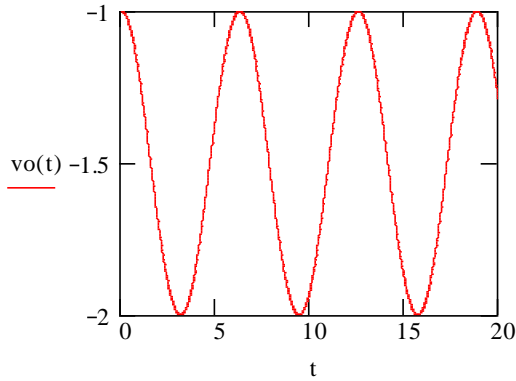

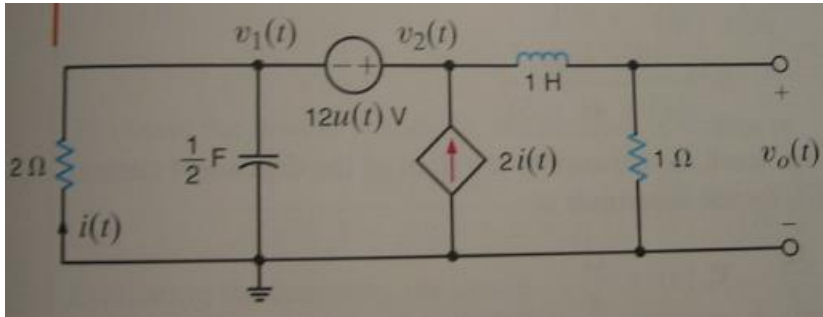Example 10: Find  $v_o(t)$ ,  $t > 0$ . Assume zero initial energy stored in the circuit at  $t=0$ .



Transformed Circuit:

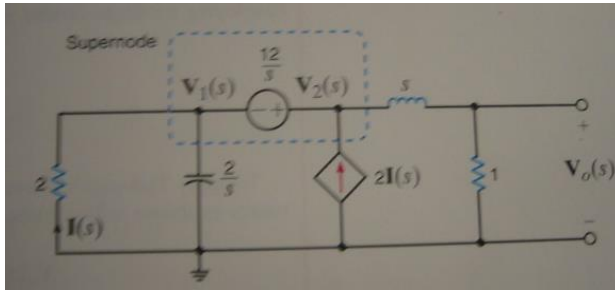

Given

$$\frac{V_1}{2} + s \cdot \frac{V_1}{2} - 2I + \frac{V_2 - V_o}{s} = 0$$

$$\frac{V_o - V_2}{s} + V_o = 0$$

$$I = \frac{-V_1}{2}$$

$$V_2 - V_1 = \frac{12}{s}$$

$$U(s) := \text{Find}(V_1, V_2, V_o, I) \rightarrow \begin{bmatrix} \frac{-24}{s \cdot (5 + 4 \cdot s + s^2)} \\ 12 \cdot \frac{(3 + 4 \cdot s + s^2)}{s \cdot (5 + 4 \cdot s + s^2)} \\ 12 \cdot \frac{(3 + s)}{s \cdot (5 + 4 \cdot s + s^2)} \\ \frac{12}{s \cdot (5 + 4 \cdot s + s^2)} \end{bmatrix}$$

$$v_o(t) := U(s)_3 \text{ invlaplace, } s \rightarrow \frac{36}{5} - \frac{36}{5} \cdot \exp(-2 \cdot t) \cdot \cos(t) - \frac{12}{5} \cdot \exp(-2 \cdot t) \cdot \sin(t)$$

